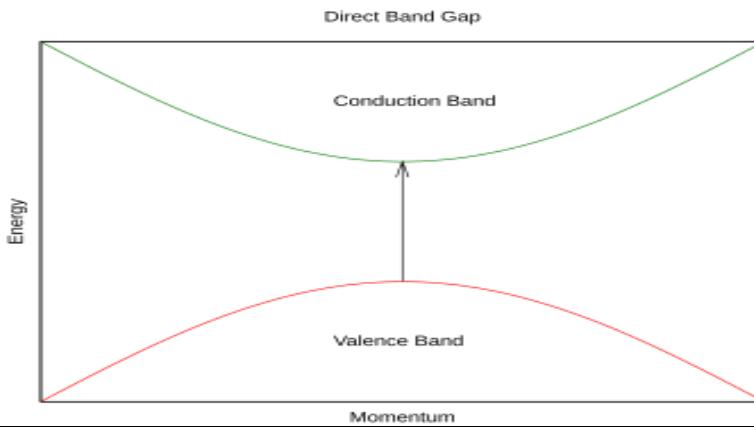



Class 12– CBSE– Physics– Chapter–Semiconductor Electronics

Max Marks – 20

Time: 40 minutes

S.No .	Questions/Problems	Mark s
1.	<p>The conductivity of a semiconductor increases with:</p> <p>(a) Increase in temperature Answer (b) Decrease in temperature (c) Constant temperature (d) None of these</p>	1
2.	<p>Assertion (A): In an n-type semiconductor, electrons are the majority carriers.</p> <p>Reason (R): Pentavalent impurities donate extra electrons to the semiconductor.</p> <p>(a) Both A and R are true, and R is the correct explanation of A. Answer (b) Both A and R are true, but R is not the correct explanation of A. (c) A is true, but R is false. (d) A is false, but R is true.</p>	1
3.	<p>Draw the energy band diagram for a p-type semiconductor. Label the valence band, conduction band, and acceptor level. Why is the Fermi level closer to the valence band in p-type semiconductors?</p> <p>Ans :</p> 	2
4.	<p>Explain the working principle of a photodiode. Draw its I-V characteristic curve for illumination and dark conditions.</p> <p>Ans : Working Principle: Photodiode operates in reverse bias. Photons generate electron-hole pairs, increasing reverse current.</p>	2

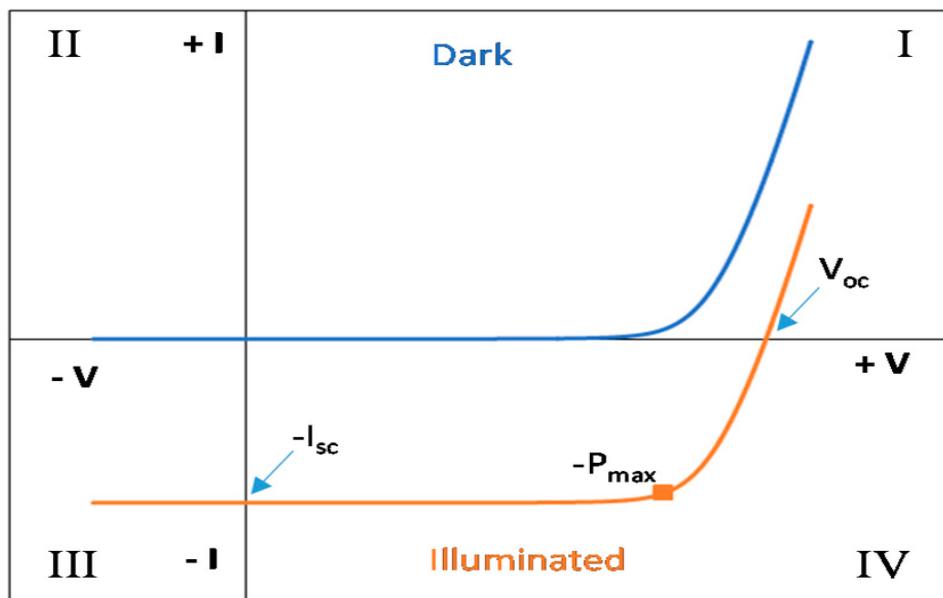


I-V Curve:

- Dark condition: Low reverse current.
- Illuminated: Higher reverse current.

5.	<p>(a) Define depletion region in a p-n junction diode. How is it formed? (b) With the help of a circuit diagram, explain how a p-n junction diode acts as a half-wave rectifier. (c) Write the expression for the average value of output voltage in half-wave rectification</p> <p>Ans : (a) Depletion Region: A region devoid of free charge carriers at the p-n junction. Formed due to diffusion of electrons and holes, creating immobile ions.</p> <p>(b) Half-wave Rectifier: AC Input → Diode (anode to p, cathode to n) → Load Resistor → Ground</p> <p>Explanation: Diode conducts only during positive half-cycle, blocking negative half-cycle.</p> <p>(c) Average Output Voltage: $V_{avg} = \frac{V_m}{\pi}$, where V_m = peak input voltage.</p>	3
6.	<p>(a) Draw the symbol and I-V characteristics of a Zener diode. (b) Explain how a Zener diode works as a voltage regulator. (c) Calculate the load voltage if a Zener diode of breakdown voltage 5.1 V is connected in parallel with a load resistor $R_L = 1\text{k}\Omega$ and the input voltage is 8 V.</p>	3



Ans : (a)

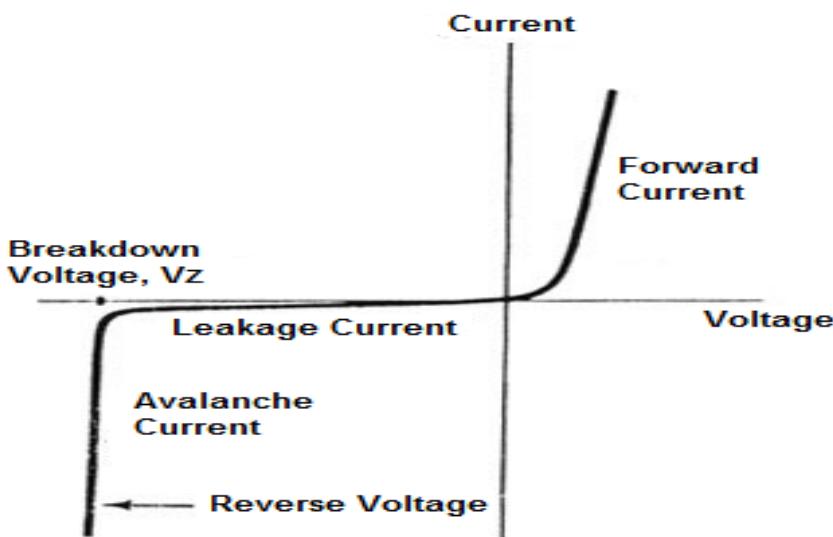Zener Diode I-V Characteristics Curve

Symbol: (Arrow indicates conventional current direction).

I-V Curve: Sharp increase in reverse current at breakdown voltage (V_Z).

(b) Voltage Regulator: Zener diode maintains constant output voltage by operating in reverse breakdown. Excess current flows through Zener, protecting load.

(c) Load Voltage: $V_L = V_Z = 5.1V$ (parallel connection).

7. (a) What is a transistor? Draw the circuit diagram of a common-emitter (CE) n-p-n transistor configuration.

4

(b) Explain transistor action with the help of arrow directions showing emitter, base, and collector currents.

(c) Derive the relation between emitter current (I_E), base current (I_B), and collector current (I_C).

(d) Define current gain (β) and write its expression.

Ans : (a) Transistor: A 3-layer semiconductor device (e.g., n-p-n).

CE Configuration Diagram:

Emitter \rightarrow Base \rightarrow Collector (Input: Base-Emitter, Output: Collector-Emitter)


(b) Transistor Action:

- Emitter injects electrons into base.

- Base (thin) allows few electrons to recombine; most diffuse to collector.

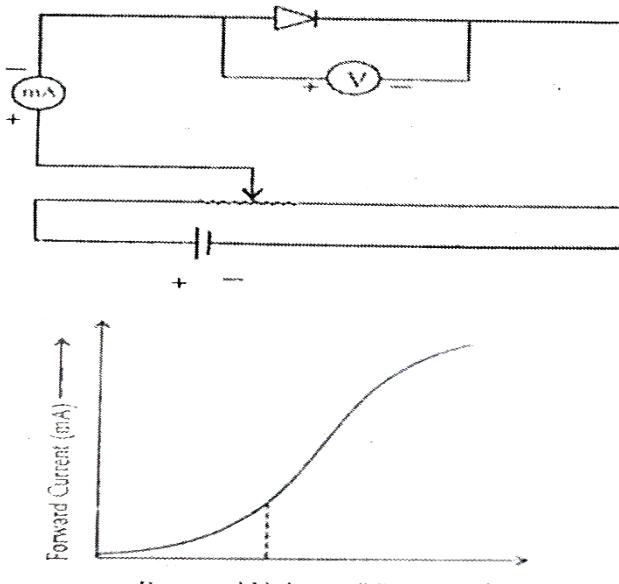
- Collector current $I_C \approx$ Emitter current I_E (since I_B is small).



	<p>Arrows: I_E into emitter, I_B into base, I_C into collector.</p> <p>(c) Relation: $I_E = I_B + I_C$.</p> <p>(d) Current Gain (β): $\beta = \frac{I_C}{I_B}$</p>	
8.	<p>Using the necessary circuit diagrams show how the V-I characteristics of a p-n junction are obtained in (i) forward biasing (ii) reverse biasing.</p> <p>Ans:</p> <p>(a) (i) p-n junction diode under forward bias:</p> <p>The V-I characteristics of p-n junction in forward bias is shown below:</p> <p>p-side is connected to the positive terminal and n-side to the negative terminal.</p> <p>Applied voltage drops across the depletion region.</p> <p>Electron in n-region moves towards the p-n junction and holes in the p-region move towards the junction. The width of the depletion layer decreases and hence, it offers less resistance.</p> <p>Diffusion of majority carriers takes place across the junction. This leads to the forward current.</p>  <p>(ii) p-n junction under reverse bias :</p> <p>Positive terminal of battery is connected to n-side and negative terminal to p-side</p> <p>Reverse bias supports the potential barrier. Therefore, the barrier height increases and the width of depletion region also increases.</p>	4



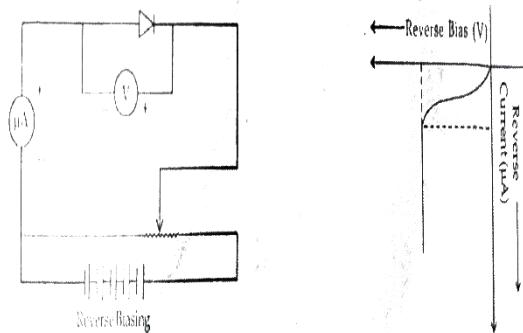Due to the majority carriers, there is no conduction across the junction. A few minority carriers cross the junction after being accelerated by high reverse bias voltage.



This constitutes a current flow in opposite direction, which is called reverse current.

The V-I characteristics of p-n junction diode in reverse bias is shown on previous page.

p-n junction diode is used as a half-wave rectifier. Its working is based on the fact that the resistance of p-n junction becomes low when forward biased and becomes high when reverse biased. These characteristics of diode is used in rectification.